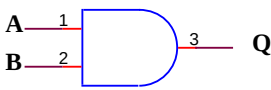
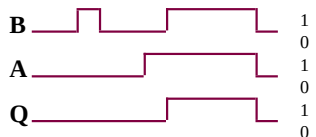
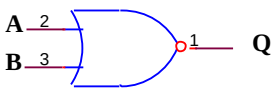
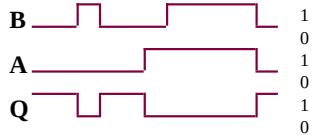
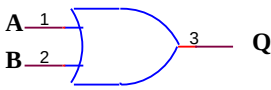
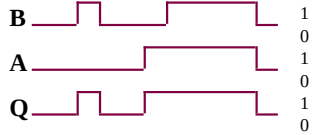
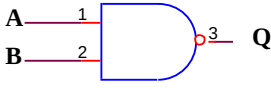
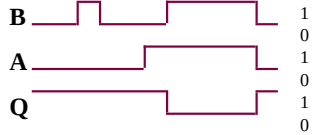
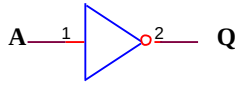


Gate - funktioner

Facitliste

Med impulsplanen som udgangspunkt, skal du finde ud af hvilken type gate, det drejer sig om.

NB: Alle de tomme felter skal udfyldes.

Navn	Diagramsymbol	Sandhedstabel	Impulsplan	Boolsk udtryk															
AND		<table><tr><th>B</th><th>A</th><th>Q</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	B	A	Q	0	0	0	0	1	0	1	0	0	1	1	1		$A * B = Q$
B	A	Q																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
NOR		<table><tr><th>B</th><th>A</th><th>Q</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	B	A	Q	0	0	1	0	1	0	1	0	0	1	1	0		$A + B = \overline{Q}$
B	A	Q																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	0																	
OR		<table><tr><th>B</th><th>A</th><th>Q</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	B	A	Q	0	0	0	0	1	1	1	0	1	1	1	1		$A + B = Q$
B	A	Q																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	
NAND		<table><tr><th>B</th><th>A</th><th>Q</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	B	A	Q	0	0	1	0	1	1	1	0	1	1	1	0		$A * B = \overline{Q}$
B	A	Q																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	
NOT		<table><tr><th>A</th><th>Q</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	Q	0	1	1	0		$A = \overline{Q}$									
A	Q																		
0	1																		
1	0																		