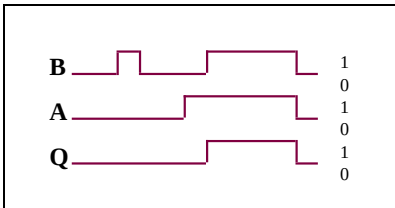
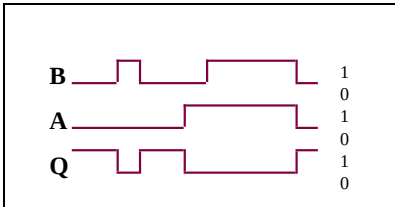
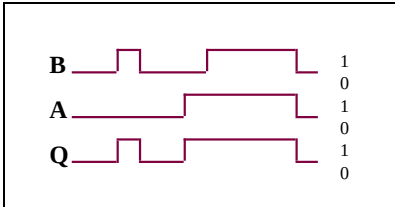
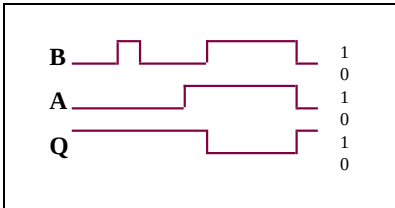
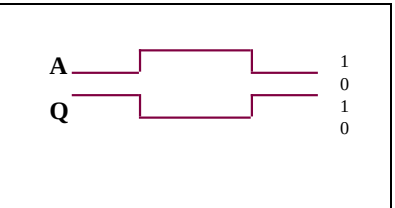


Rutineopgave:

Gate - funktioner

Med impulsplanen som udgangspunkt, skal du finde ud af hvilken type gate, det drejer sig om.
NB: Alle de tomme felter skal udfyldes.

Navn Diagramsymbol Sandhedstabel Impulsplan Boolsk udtryk

		<table><tr><th>B</th><th>A</th><th>Q</th></tr><tr><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td></td></tr></table>	B	A	Q	0	0		0	1		1	0		1	1			
B	A	Q																	
0	0																		
0	1																		
1	0																		
1	1																		
		<table><tr><th>B</th><th>A</th><th>Q</th></tr><tr><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td></td></tr></table>	B	A	Q	0	0		0	1		1	0		1	1			
B	A	Q																	
0	0																		
0	1																		
1	0																		
1	1																		
		<table><tr><th>B</th><th>A</th><th>Q</th></tr><tr><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td></td></tr></table>	B	A	Q	0	0		0	1		1	0		1	1			
B	A	Q																	
0	0																		
0	1																		
1	0																		
1	1																		
		<table><tr><th>B</th><th>A</th><th>Q</th></tr><tr><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td></td></tr></table>	B	A	Q	0	0		0	1		1	0		1	1			
B	A	Q																	
0	0																		
0	1																		
1	0																		
1	1																		
		<table><tr><th>A</th><th>Q</th></tr><tr><td>0</td><td></td></tr><tr><td>1</td><td></td></tr></table>	A	Q	0		1												
A	Q																		
0																			
1																			